



TED (21) -3044
(Revision- 2021)

N22-2110220227B

Reg.No.....
Signature.

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/MANAGEMENT/
COMMERCIAL PRACTICE – NOVEMBER - 2022**
DIGITAL ELECTRONICS

(Maximum Marks : 75)

[Time : 3 hours]

PART-A

I. Answer all the following questions in one word or one sentence. Each question carries 1 mark.

(9x1=9 marks)
Module Outcome Cognitive level

| | | | |
|---|---|--------|---|
| 1 | Hexadecimal value of decimal 21 is..... | M 1.01 | U |
| 2 | Write the 1's complement of 1010 | M 1.01 | U |
| 3 | Write any one universal logic gate and show its symbol. | M1.03 | R |
| 4 | Name the fastest logic family. | M2.02 | U |
| 5 | Number of control signals required for a 4x1 Multiplexer is..... | M2.04 | U |
| 6 | Name the type of logic circuit in which the output depends upon only the present input and present state. | M3.01 | U |
| 7 | Serial in serial out shift register has.....input line and output line. | M3.03 | U |
| 8 | Counter without common clock is called.....counter. | M4.01 | U |
| 9 | Name the memory which is also called volatile memory. | M4.04 | R |

PART - B

II. Answer any Eight questions from the following. Each question carries 3 marks.

(8x3=24marks)
Module Outcome Cognitive level

| | | | |
|---|---|--------|---|
| 1 | Add the following Hexadecimal numbers. a) AC6 + 9B b) B59 + 64 | M 1.01 | U |
| 2 | Show the conversion of NAND gate to AND and NOT gates. | M 1.03 | U |
| 3 | Reduce the expression $Y = \sum m (0,2,3,4,5)$ using K Map. | M1.04 | A |
| 4 | Write any three features of TTL logic family. | M2.02 | U |
| 5 | Show the functional diagram and logic diagram of logic circuit to select one data line at a time from two input data lines. | M2.04 | A |
| 6 | Draw the logic of a 4 bit Ripple Carry Adder. | M2.04 | U |
| 7 | Draw the logic symbol and truth table of T flip flop. Mention its applications. | M3.02 | U |
| 8 | Draw the logic diagram of 3 bit ring counter using D flip flops. | M3.04 | U |



| | | | |
|----|---|-------|---|
| 9 | Write any three features of Asynchronous counter. | M4.01 | U |
| 10 | Differentiate PROM, EPROM. | M4.04 | U |

PART - C

Answer **all** questions from the following. Each question carries 7 marks.

(6x7=42marks)

| | | Module Outcome | Cognitive level |
|-----------|---|----------------|-----------------|
| III | Perform the following operations. (i) Multiply 1011_2 by 110_2 (ii) 46-14 using 8 bit 2's complement method. (iii) Convert $2AB_{16}$ to binary. | M1.01 | U |
| OR | | | |
| IV | Minimize the following expression using K Map $F(A,B,C) = \sum m(1,4,7,10,13) + \sum d(5,14,15)$ | M1.04 | U |
| V | Using K Map design a 2 bit Gray to Binary code converter. | M2.04 | U |
| OR | | | |
| VI | Explain 3 line to 8 line Decoder using truth table only. | M2.04 | U |
| VII | With the help of conversion table and K Map show the conversion of JK flip flop to T flip flop. | M3.02 | A |
| OR | | | |
| VIII | With necessary diagrams explain 3 bit Johnson counter using D flip flops. | M3.04 | U |
| IX | Explain JK flip flop with logic diagram. Mention its truth table. | M3.02 | U |
| OR | | | |
| X | With a diagram explain the working of Serial in - Parallel out Shift register. | M3.03 | U |
| XI | With the logic diagram and timing diagram briefly explain a two bit ripple up counter with positive edge triggering | M4.02 | U |
| OR | | | |
| XII | Write short notes on Random Access Memory. | M4.04 | U |
| XIII | Design and implement a mode 6 Asynchronous counter using T flip flops. | M4.02 | A |
| OR | | | |
| XIV | Design a 3 bit synchronous up counter. (Excitation table and design equations need, no need to implement) | M4.03 | A |
